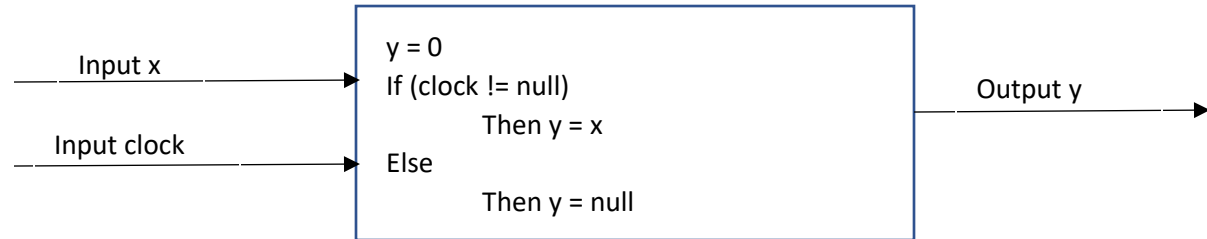


SE-410 Homework 7

Cameron Stark

1.)



2.)

The input-output behavior of the above component is the output of the input x if the clock exists and a null output if the clock does not exist as an input. Which defines that component is reliant on the existence of the clock.